

MODULE 4 – PIPELINE ADCS

JULY 2025

RENESAS ELECTRONICS CORPORATION

AGENDA


- Start from the 4-bit SAR ADC designed on the previous module workshop.
- Move from there to understand the SAR architecture limitations.
- Get into Pipeline ADC architectures and understand how it overcomes the SAR limitations.
- Practical examples to understand key design aspects from the pipeline architecture:
 - Residue Amplification and Inter-Stage Gain
 - Digital Correction
 - Effects of the STG1 Capacitors Mismatch on the ADC DNL/INL



A PRACTICAL PERSPECTIVE ON PIPELINE ADCS


SAR ADC TIMING (EXAMPLE BASED ON THE WORKSHOP)

 4-bit SAR-ADC @ 80MS/s (Workshop Exercise)




Insert additional bits

12-bit SAR-ADC @ 80MS/s

 


Increase the sampling frequency

4-bit SAR-ADC @ 160MS/s

 


 PIPELINE ADC TIMING (EXAMPLE BASED ON THE WORKSHOP)




- STG1 quantizes 4-bit and amplifies the residue voltage (V_{res}) → STG1 reaches 120MS/s operating frequency.
- STG2 gets an extended time slot for quantization.
(due to reduced duty cycle on STG2 sampling phase, which matches STG1 amplification phase).
- STG2 manages to quantize 16-bit with the extended time slot it has available (optimistically considering the average easy decisions time would be maintained... while in practice it would not happen, because STG2 V_{res} is much smaller, therefore the comparator's decisions will be slower).
- Being more realistic... it is reasonable to think STG2 may be able to quantize ~9 bit @120MS/s.
- Summing STG1 and STG2 bits (with 1-bit redundancy) results in a 12-bit ADC @ 120MS/s

 
PIPELINE ADC STRUCTURE (2 STAGES, EXAMPLE)



Digital Correction Operation:

 


 PIPELINE ADC STRUCTURE (N STAGES, GENERIC)




The stages quantization does not need necessarily to be SAR based.
It can be Flash based, or TDC based, or any other type.

 
Digital Correction Operation (Multi-Stage example):



 
4-BIT STG1 TRANSFER FUNCTION – VRES (VIN)



 4-BIT STG1 AMPLIFIED TRANSFER FUNCTION - VRES_AMP(VIN)



 COMPARING VRES AND VRES_AMP – THE NOISE ADVANTAGE




PIPELINE NOT ONLY FASTER BUT ALSO MORE POWER EFFICIENT

Pipelining → good power-efficiency for noise
SAR ADC → good power-efficiency for large signals


ISSCC2014 – BROADCOMM PAPER

 Required Energy to bring down Noise Level




Multiple high-energy (low-noise) events
SAR-assisted pipelined ADC can do better !

 Required Energy of SAR-assisted Pipelined ADC







Low noise level is required only once
1 high-energy event: increased power efficiency wrt SAR




 
RESIDUE VOLTAGE AMPLIFICATION AND INTER-STAGE GAIN (ISG)



    EXCESS ISG ERROR AND ITS INFLUENCE ON THE ADC LINEARITY




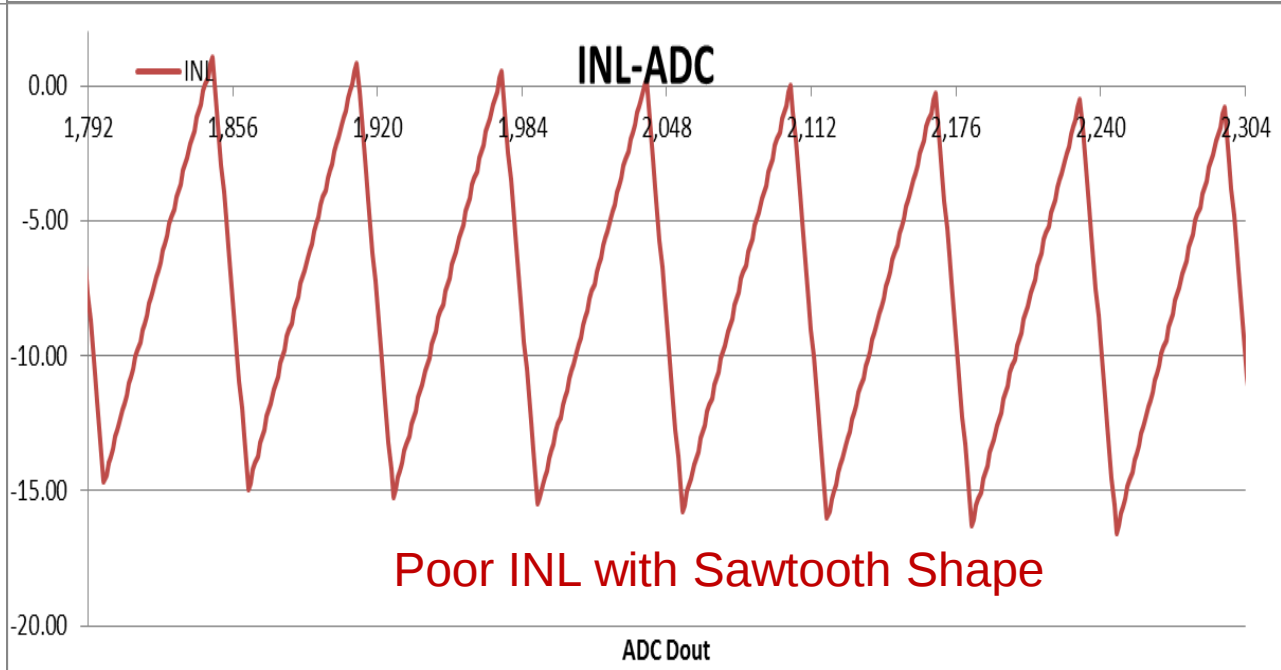   REDUCED ISG ERROR AND ITS INFLUENCE ON THE ADC LINEARITY



OVER-RANGE (OVR) DEFINITION

4-bit STG2
(as example)

 

THE DIGITAL CORRECTION OPERATION

- The ADC output code (D_{OUT}) is computed by the Digital Correction Circuit, combining the different stages bits.
- For a Two-Stage Pipeline ADC (mid-rise) the Digital correction equation is the following:


$$D_{OUT} = 2^{(N2-1)} \cdot code_{STG1} + code_{STG2} - 2^{(N2-2)}$$

- In the example of the workshop, we have $N1=4$ -bit and $N2=4$ -bit, so we get:

$$D_{OUT} = 8 \cdot code_{STG1} + code_{STG2} - 4$$


- Next slide we check an example on how the digital correction and the inter-stages redundancy bit works to correct STG1 quantization code errors.

 4-BIT STG1 + 4-BIT STG2 EXAMPLE OF THE DIGITAL CORRECTION MAGICS



RESIDUE AMPLIFICATION APPROACHES





Residue Amplifier

 

	Closed-Loop	Open-Loop	Open-Loop + Calibration
Gain Accuracy	😊	😞	😊
Linearity	😊	😞	😊
Speed	😞	😊	😊
Efficiency	😞	😊	😊
Stability	😞	😊	😊
Scaling Friendly	😞	😊	😊

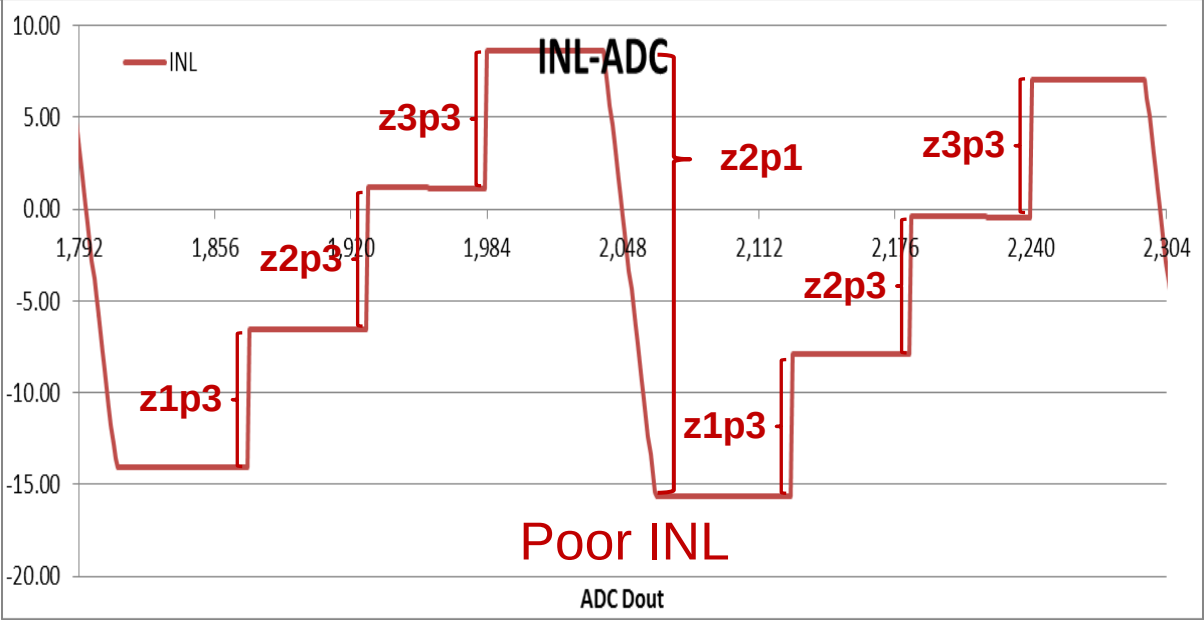  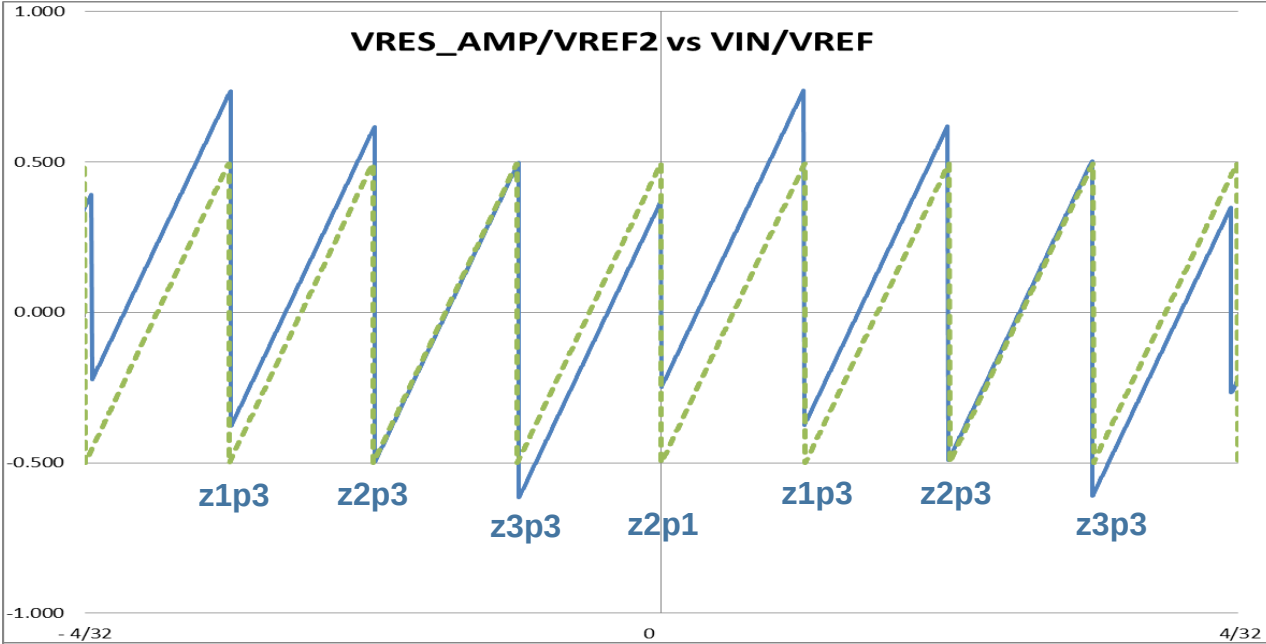[B. Murmann, JSSC, 2003]

EFFECT OF THE STG1 DAC CAPACITORS MISMATCH ON THE ADC LINEARITY (6-BIT STG1)





marco.rodriques.ue@renesas.com

**Send us your questions.
We are glad to help you.
Thank you!**